



Harmonics and Noise in Photovoltaic (PV) Inverter and the Mitigation Strategies



Example of a PVI 82KW-480 VAC inverter

PV inverters use semiconductor devices to transform the DC power into controlled AC power by using Pulse Width Modulation (PWM) switching. PWM switching is the most efficient way to generate AC power, allowing for flexible control of the output magnitude and frequency. However, all PWM methods inherently generate harmonics and noise originating in the high dv/dt and di/dt semiconductor switching transients. In order to reduce harmonics and switching noise, external filtering needs to be added.

The PWM waveform is generated by comparing a reference signal (sinusoidal red trace) and a carrier waveform (triangular blue trace). The PWM waveform controls the Insulated Gate Bipolar Transistor (IGBT) switches to generate the AC output. When the reference signal is bigger than the carrier waveform, the upper IGBT is triggered

STEELMAN INDUSTRIES, INC.

Built to last since 1957!

Rotary Phase Converters

- Provides 3-Phase Power When Only Single Phase Service is Available
- Single or Multi-Motor Applications
- Available in Indoor (ODP) and Outdoor (TEFC) Models

Steelman Industries, Inc.
2800 Hwy. 135 (P.O. Box 1461)
Kilgore, TX 75662
800.337.5827 • 903.984.1384 fax
www.steelman.com

Visit us at: www.steelman.com

ARPI of USA™
AUTOMATED RECYCLING PRODUCTS INCORPORATED

"A New World Of Resources By Recycling"

POWER WIRE STRIPPER™

<p>COMC 14awg - 600mcm</p>	<p>RES 16awg - 250mcm</p> <p>Processes up to 4,200 feet per hour.</p> <p>Strips plastic coated electrical wire safely, economically and easily.</p>
<p>DRM Drill Powered Wire Stripper</p>	<p>New SEP5 SepShear</p> <p>Separates and shears the aluminum or copper outer layer of bare ACSR cable, while leaving the steel center core in full length.</p>

866-804-3829 • www.arpiusa.com

Visit us at: www.arpiusa.com

on (lower IGBT being off) and positive DC voltage is applied to the inverter output phase (A). In the other case, when the reference signal is smaller than the triangular carrier waveform, the lower IGBT is turned on (upper IGBT being off) and negative DC voltage is applied to the inverter output. The reference signal magnitude and frequency determine the amplitude and the frequency of the output voltage. The frequency of the carrier waveform is called the modulation frequency. In order to generate more precise sinusoidal AC voltage waveforms and keeping the size of the LC filter small, high modulation frequencies are generally used.

There are many industrial standards that control the noise and harmonic contents for AC motor drives, Uninterrupted Power Supplies (UPS) or other AC power applications. In the case of grid-tied PV inverters, the Institute of Electrical and Electronics Engineers (IEEE) 1547, Underwriters Laboratories (UL) 1741 and FCC Part 15B standards specify the guidelines to control the harmonic contents of the output current and the Electro Magnetic Interference (EMI) generation in the inverter. The guidelines guarantee that:

The inverters do not generate excessive noise and harmonics, which can contaminate the AC grid voltage.

The inverters are immune to electrical and magnetic noise from other sources and provide reliable operation in an environment of high electromagnetic noise.

The inverters do not generate unwanted radiated or conducted noise, which can disturb the stable operation of other equipment coupled either electrically or magnetically.

Most of the PV inverters manufactured in the United States are designed to meet UL 1741 and IEEE 1547 standards. As the capacity of PV generation in power distribution systems grows, utility companies become increasingly concerned that the noise and harmonics from the PV inverter systems might adversely impact the power quality or affect the operation of other equipment and cause it to malfunction or otherwise disrupt the stable operation of the power distribution system.


This article lists the possible sources of the harmonics and switching noise generated by the PV inverter and describes how they can be controlled to meet customer requirements and relevant industrial stan-

dards. To present the theoretical and experimental analysis of this phenomenon, a Solectria Renewables PVI 82KW - 480VAC PV inverter system is being used. However, since most PV inverters have similar types of component configurations, the information in this article can be used to understand the harmonics and EMI issues in a variety of inverter systems.

PV Inverter System Configuration

A Solectria PVI 82KW inverter include filters used for attenuating the high frequency noise on the inverter output voltages and currents. There are two main sources of high frequency noise generated by the PWM inverters. The first one is the PWM modulation frequency (2 ~ 20kHz). This

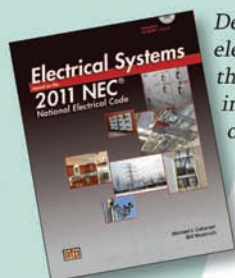NEC® Training Materials Applying the New Code with Confidence




Designed for use by journeyman and master electricians, inspectors, contractors, and others, this authoritative textbook is recognized in the industry for providing a comprehensive overview of the NEC®.



This new textbook covers the major changes contained in the 2011 NEC®. The textbook is also available in an electronic format.



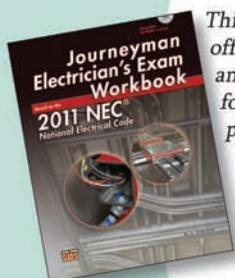This extremely practical workbook offers an overview of the exam and realistic examples involving formulas, NEC®-related problems, and definitions.



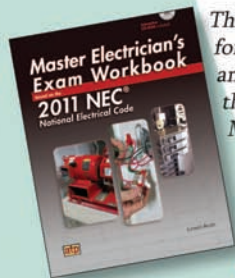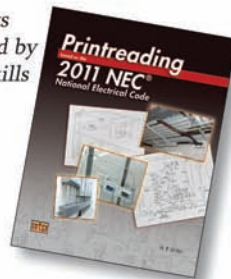This new edition maintains its status as the industry standard by incorporating printreading skills and relevant NEC® topics.



This new workbook is designed for electricians-in-training and experienced journeymen to thoroughly prepare to pass the Master Electrician's Exam.

**Visit us at the 2011 NECA Show
booth #1835**



AMERICAN TECHNICAL PUBLISHERS
10100 Orland Parkway, Ste. 200 • Orland Park, IL • 60467-5756
708.957.1100 • Fax: 708.957.1101 • 800.323.3471

NEC is a registered trademark of the National Fire Protection Association, Inc.

Scan here to
access
go2atp.com



Visit us at: www.americantech.net



component is mainly attenuated by the LC filter and the transformer. The second source originates from the switching transients of the power electronics switching devices (IGBTs). The frequency of the switching transients is dependent on the device switching characteristics, gate drive circuit and the snubber circuit in the inverter, and ranges from several hundred kHz to 100MHz. The series filter and the shunt filter are designed to attenuate the frequency components caused by these switching transients and also the harmonics from other subsystem components such as the switched mode power supply (SMPS) and other inverter control circuitry.

Most of the harmonic components in the voltage and current waveforms are filtered out by the LC, series and shunt filters. The inverter output current is in phase with the voltage (unity power factor) and the total harmonic distortion (THD) is less than 5% at rated operation, which is far better than the current THD of most industrial loads, and is comparable to the output current waveforms of an Uninterruptable Power

Supply (UPS).

PWM Frequency and LC Filter

An LC filter is used to attenuate the PWM modulation frequency and its harmonics in the inverter system. The leakage inductance of the integrated isolation transformer further attenuates the high frequency component so that the output current will be sinusoidal and meet the desired THD limit. A symmetrical PWM scheme is generally preferred to reduce the ripple in the inverter output current. A symmetrical PWM scheme compared to an asymmetrical PWM reduces the effective peak-to-peak ripple current by half when using the same switching frequency.

An inverter's power stage output voltage waveform is composed of a series of square waveforms and includes high frequency components. The current waveform is relatively smooth and sinusoidal as the inverter output current flows into the inductor such that it cannot change instantaneously.

In the time domain, the waveforms do

not look very different. However, the Fast Fourier Transformation (FFT) results show that the inverter current after the LC filter has much less high frequency components than the unfiltered power stage output current.

This filtering effect can be illustrated in a Bode Plot. The LC filter frequency characteristics use the theoretical frequency analysis and measured harmonic components with a frequency analyzer when the inverter operates at full power.

High Frequency Noise Generated by Switching Transients

When the switching devices are turned on and off, high dv/dt and di/dt cause oscillations during the transients, which contain high frequency noise in the range of 100kHz or higher.

By using a slow switching transient, the oscillation can be reduced but switching losses are increasing due to longer operation of IGBTs in the active region. With a faster switching speed, the switching losses can be kept lower but oscillations in volt-


Get Cool!




Extend transformer life!

Increase transformer capacity up to 166%!

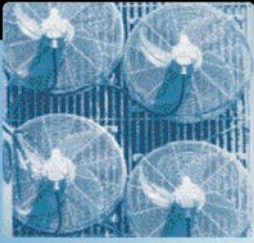- expert technical assistance
- low sound levels
- energy-efficient motors
- large inventory
- one-piece cast aluminum blades
- galvanized or stainless steel guards





KRENZ-VENT

quality engineered, performance tested

p.o. box 187 germantown, wisconsin 53022


262.255.2310


www.krenzvent.com

Visit us at: www.krenzvent.com

Weather Resistant Solid Brass Padlocks

Made to your specifications in the U.S.A.





Hercules Industries, U.S.A. ®

HERCULES INDUSTRIES, INC.

Manufacturer of HERCULOCK Padlocks

P.O. Box 197 • Prospect, Ohio 43342

Toll Free: 1-800-345-2590

Fax: (740) 494-2274

www.HERCULOCK.com

Visit us at: www.herculock.com

34 The Electric Current August/September 2011

Since the DC voltage control loop bandwidth is low, it does not cause any harmonics or EMI issues.

age and current are being generated due to the parasitic inductance and capacitance in the inverter stack. This high frequency oscillation may fall into the frequency band regulated by FCC. In order to increase the overall efficiency of the inverter and at the same time to minimize EMI, the IGBT switching speed and noise filter design must be carefully coordinated.

There are other sources of switching noise in the inverter system caused by the Switch Mode Power Supplies (SMPS) and the digital control logic circuits. The noise from these components can reduce the system performance by contaminating internal analog feedback signals, resulting in logic level or communication errors and could also cause EMI interference with the outside world.

The high frequency noise can be classified into radiated noise and conducted noise. The radiated noise can be controlled in many ways at the board level and at the system level such as shielding, component layout, wiring routing, and signal grouping. The conducted noise can be controlled by grounding or the use of proper filters, carefully designed to eliminate specific frequency components. In Solectria's PVI 82KW inverter, excellent noise levels were achieved by implementing a robust printed circuit board (PCB) layout in combination with hardware and software filters. Noise in signal circuits is controlled by ferrite beads and proper grounding. The PVI 82KW inverter also features series and shunt filters in the final output stage of the system. These filters are band limiting and designed to filter out switching transient frequencies.

Series Filter

The series filter in the PVI 82KW attenuates both common mode and differential mode noise. It provides 80dB common mode attenuation for the frequencies between 100kHz and 1MHz, and 70dB differential mode attenuation for the frequencies between 200kHz and 3MHz. The filter is selected to eliminate the system specific dominant frequency components, and is not active in the lower PWM modulation frequency range.

Shunt Filter

The selected shunt filter for the PVI 82KW inverter has a resonance point around 150kHz and provides a reduction of noise interference particularly in the fre-

quency range between 50kHz and 5MHz. This filter is added to further reduce the switching noise from the power stage as well as from the switch mode power supply in the inverter control system. The shunt filter also provides a protection circuit against surges of atmospheric origin to the grid, typically caused by lightning and characterized by high current levels of short duration. The filter reacts in a few microseconds to current spikes of a few kA, and protects the system against impulse surges of up to 1000 volts.

System Wide EMI Control

Some of the EMI reduction strategies that are used in a PVI 82KW inverter include:

- Solid Grounding
- Controlled Wire Routing
- Board level filtering and EMI reduction layout
- Wire twisting
- Stack configuration for reduced stray inductance
- Power electronics for EMI shielding
- Analog signal conditioning using ferrite beads
- DC side high power wiring for EMI shielding

Harmonics Generated by Firmware Control

Conventional PV inverters firmware runs at least two nested control loops. One is the AC current control loop to control the inverter output current, purely sinusoidal and in phase with the grid voltage, generating active power. The other is the DC voltage control loop in conjunction with a Maximum Power Point Tracking (MPPT) algorithm to most efficiently harvest the DC power generated by the solar panels.

When grid conditions change due to power grid transients, power line faults or load based voltage fluctuations in the distribution line, the inverter output current is controlled to balance the power transfer from the PV array to the grid. The current control loop gains need to be tuned properly, so that the firmware does not generate frequency oscillations, which in turn

would generate harmonics in the 100 ~ 1kHz range. The DC voltage control loop is around the current control loop and is usually controlled at a lower sampling rate. If the DC voltage fluctuates due to sudden changes in weather conditions, the DC voltage control loop has a certain bandwidth to react and stabilize the system output. During sunlight transients, the system might generate even slower oscillations in the DC bus and output AC currents.

Since the DC voltage control loop bandwidth is low, it does not cause any harmonics or EMI issues. However, if the voltage control loop were not tuned properly, the generation efficiency would decrease due to failure to track the maximum power point of the PV panels.

Solectria Renewables' inverters have been fully tested at different load conditions to have excellent dynamic characteristics for both the AC current and DC voltage control loops. The AC current control bandwidth is about 2kHz and the DC voltage control bandwidth is less than 100Hz.

Conclusion

This article described how the current harmonics and EMI are controlled in PV inverters. IEEE 1547, UL 1741 and FCC Part 15B standards impose strong guidelines for grid-tied PV inverters to reduce current harmonics and eliminate electromagnetic noise. Extra attention is given by the PV inverter manufacturer to design inverters that are immune to EMI problems and guarantee reliable operation of the inverter in all worst case operating conditions.

Different types of practical harmonics and noise reduction strategies for a commercial three-phase PV inverter were introduced in this article. The filtering of harmonics and EMI needs to be carefully designed to maintain the control bandwidth of the inverter and to provide clean and reliable control signals in both analog and digital electronic circuits. The PVI 82KW inverter system is equipped with several levels of harmonics and EMI filtering and its effectiveness and reliability have been proven in harshest commercial and utility scale applications. □

Article written by **Dr. Soonwook Hong**, Senior Electronic Power Systems Engineer and **Michael Zuercher-Martinson**, Chief Technology Officer of Solectria Renewables, LLC.

For more information, please go to www.solren.com.



RESIDENTIAL SOLUTIONS 1.8 TO 15KW

Solectria Renewables, LLC is the leading U.S. based grid-tied photovoltaic inverter manufacturer for residential, commercial and utility-scale solar installations. Our versatile line of high efficiency products provide power solutions ranging from 1 kW residential systems to multi-megawatt solar farms. Solectria Renewables' products are backed by more than 30 years of experience in the power electronic and inverter industries and supported by world class warranties. All of our commercial and utility-scale PV inverters are manufactured in the USA, ARRA compliant, Ontario FIT Content Compliant, and listed to UL 1741/IEEE 1547.



Built for the real world

REAL WORLD SOLUTION: Magnani Residence

Size: 5 kW

Installer:  solarflair

Location: Framingham, MA

Products: PVI 5000

"We have partnered with and chosen Solectria Renewables' residential inverters for various installations since 2005. Their residential inverters are the most efficient and reliable in the grid-tied PV market."

– **Matt Arner**, President and Certified NABCEP PV Installer, SolarFlair Energy, Inc.

